



$$\frac{1}{R_T} = \frac{1}{R_L} + \frac{1}{R_R} = \frac{1}{26} + \frac{1}{130}$$

$$R_T = 21.6 \Omega$$

