



READING ON THE VOM = ??

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_x}$$

$$R_T = 1.33\bar{3}\Omega \quad \frac{1}{R_T} = \frac{1}{2} + \frac{1}{4} = .75$$

$$R_T = \frac{1}{.75}$$

$$\frac{1}{R_T} = \frac{0.75}{1}$$

$$I = R_T \left(\frac{0.75}{\cancel{0.75}} \right)$$